

# Assignment 5 and 6



Deadline: Thursday 16/5/2017 12 pm

Question 1 and 2 is Assignment-5 while Question-3 is Assignment 6

1. Draw the waveform of Following 2 Designs (.5 + .5 = 1 Weightage)

Note:  $V_{dd}$  in 1<sup>st</sup> figure means 5 V (high) and "Logic 1" in 2<sup>nd</sup> figure means 5 V (HIGH)


*A four-bit "up" counter*

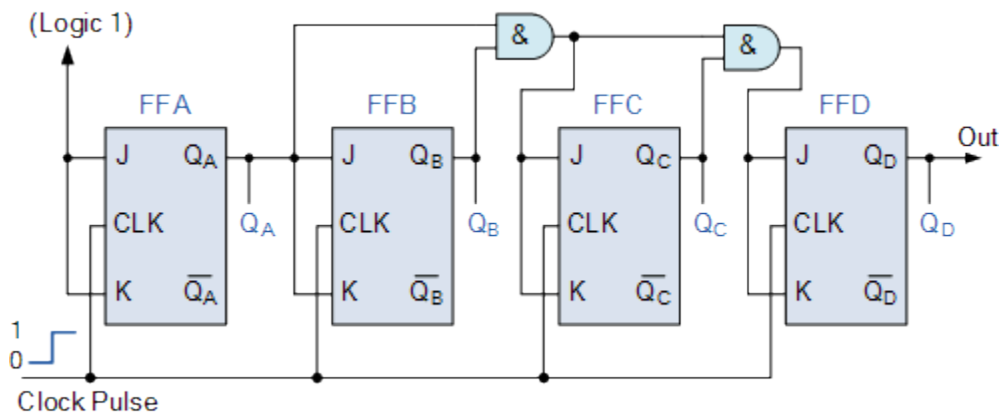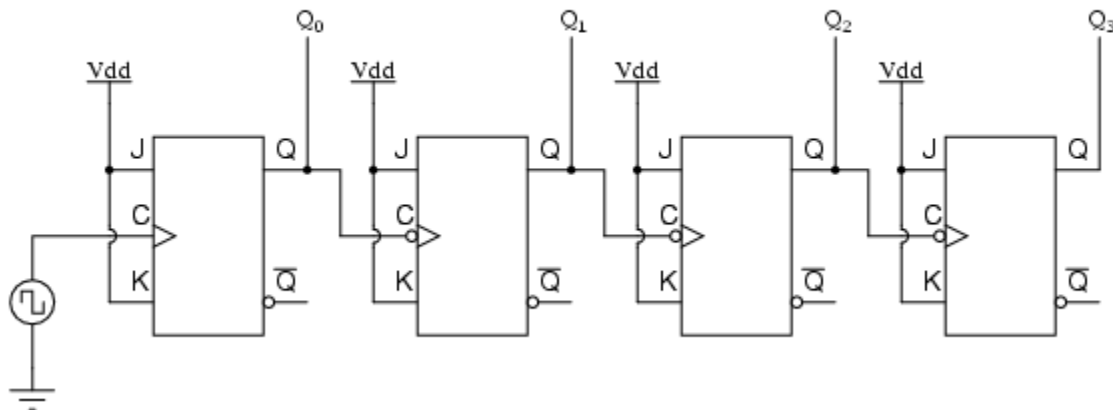

2. Design synchronized counter for Following Sequence. (.5 + .5 = 1 Weightage)

a. Using J-K Flip Flops (.5 weightage)

b. Using D Flip Flops (.5 weightage)

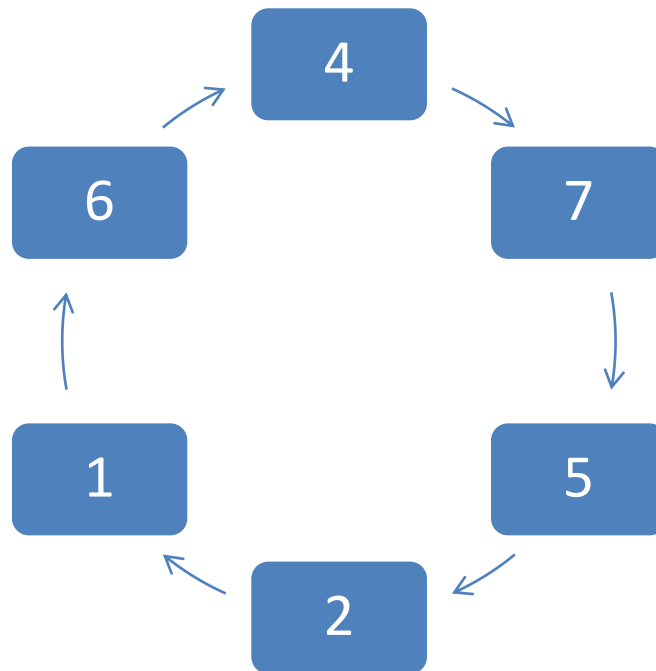

3. Design UP/DOWN synchronized counter for Sequence given in Q2. (2 Weightage)